

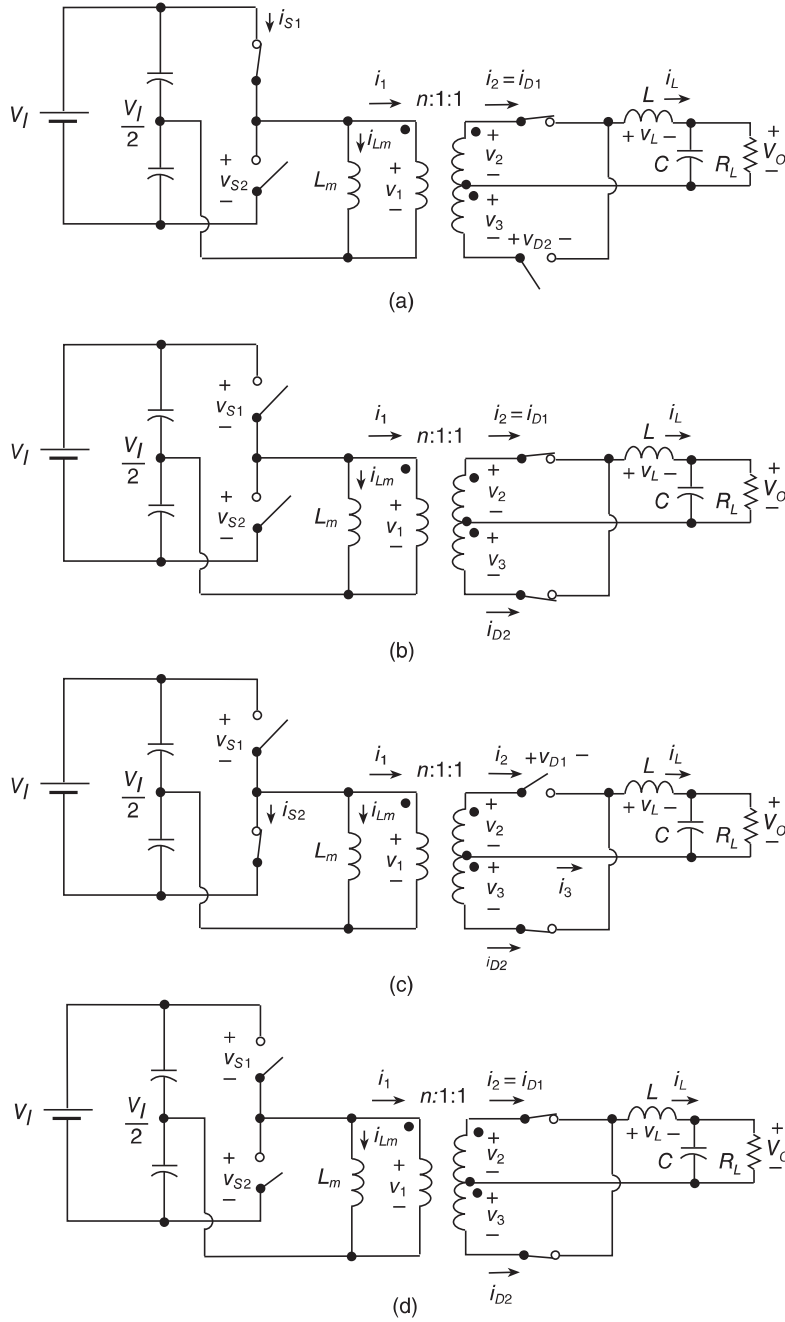


Figure 7.3 Equivalent circuit of the half-bridge converter with a transformer center-tapped rectifier for CCM. (a) For $0 < t \leq DT$. (b) For $DT < t \leq T/2$. (c) For $T/2 < t \leq T/2 + DT$. (d) For $T/2 + DT < t \leq T$.